

## Homework09

8. Design a circuit for a light fixture controlled by four switches, where flipping one of the switches turns the light on when it is off and turns it off when it is on.

12.3 ex. 8 Suppose the first switch is  $x$  second is  $y$  third is  $z$  fourth is  $w$  1 represent the switch is open 0 represent the switch is off when light is on  $F(x,y,z,w) = 1$  when light is off.


$$F(x,y,z,w) = 0$$

suppose when four switch is off the light is off.

To turn on the light, you need to turn on one or three switch

| $x$ | $y$ | $z$ | $w$ | $F$ |
|-----|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   | 0   |
| 1   | 0   | 0   | 0   | 1   |
| 0   | 1   | 0   | 0   | 1   |
| 0   | 0   | 1   | 0   | 1   |
| 0   | 0   | 0   | 1   | 1   |
| 1   | 1   | 0   | 0   | 0   |
| 1   | 0   | 1   | 0   | 0   |
| 1   | 0   | 0   | 1   | 0   |
| 0   | 1   | 1   | 0   | 0   |
| 0   | 1   | 0   | 1   | 0   |
| 0   | 0   | 1   | 1   | 0   |
| 1   | 1   | 1   | 0   | 1   |
| 1   | 1   | 0   | 1   | 1   |
| 1   | 0   | 1   | 1   | 1   |
| 0   | 1   | 1   | 1   | 1   |
| 1   | 1   | 1   | 1   | 0   |
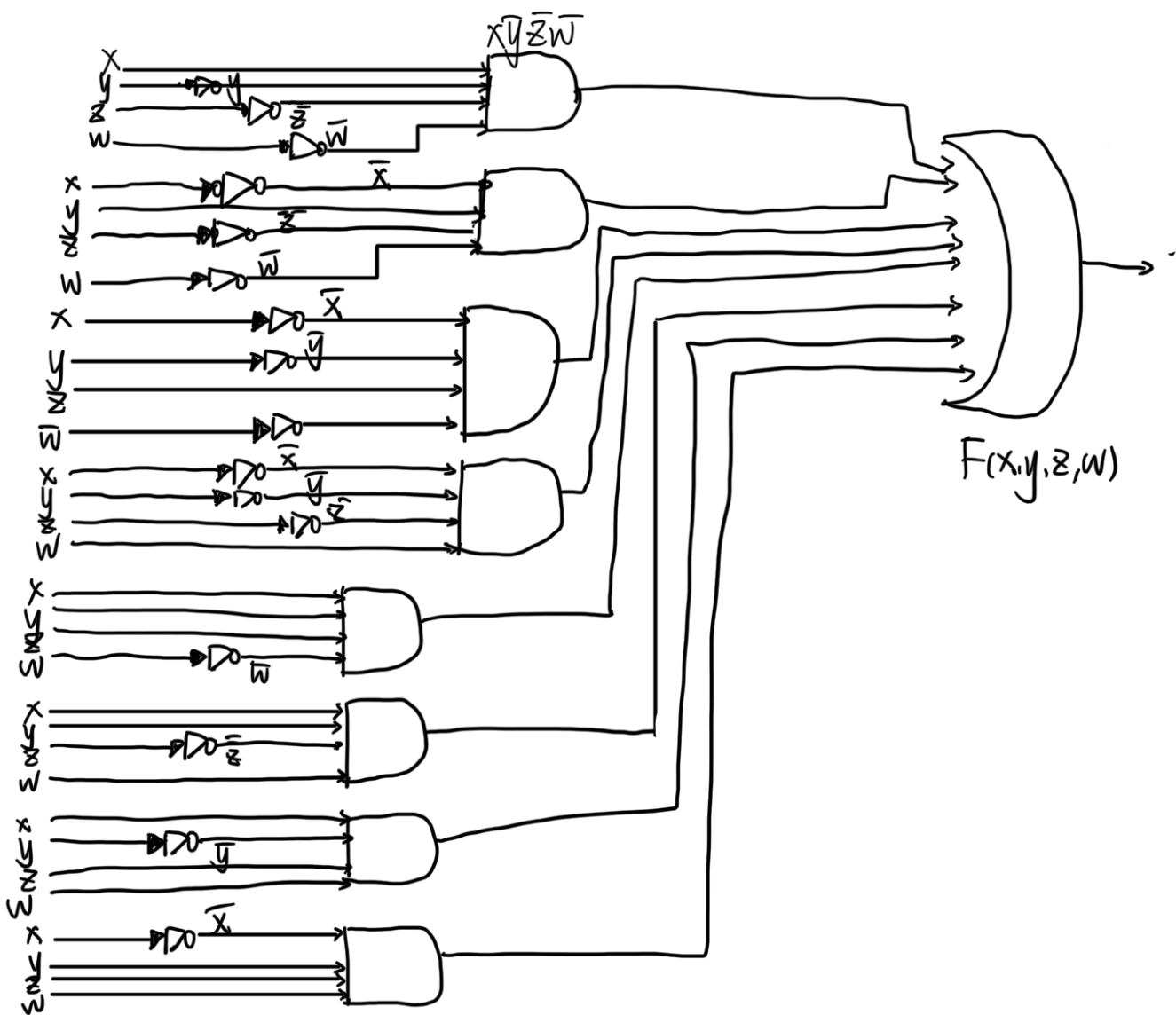
$$F(x,y,z,w) = x\bar{y}\bar{z}\bar{w} + \bar{x}y\bar{z}\bar{w} + \bar{x}\bar{y}z\bar{w} + \bar{x}\bar{y}\bar{z}w + x\bar{y}\bar{z}w + x\bar{y}z\bar{w} + \bar{x}yz\bar{w} + \bar{x}y\bar{z}w$$




10. Construct a circuit for a half subtractor using AND gates, OR gates, and inverters. A **half subtractor** has two bits as input and produces as output a difference bit and a borrow.

12.3 ex.10 Suppose output bit is  $z$ , borrow is  $w$

| $x$ | $y$ | $z$ | $w$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 1   | 0   | 1   | 0   |
| 0   | 1   | 1   | 0   |
| 1   | 1   | 0   | 1   |

$$z = (x+y)(\overline{xy})$$

$$w = \overline{xy}$$

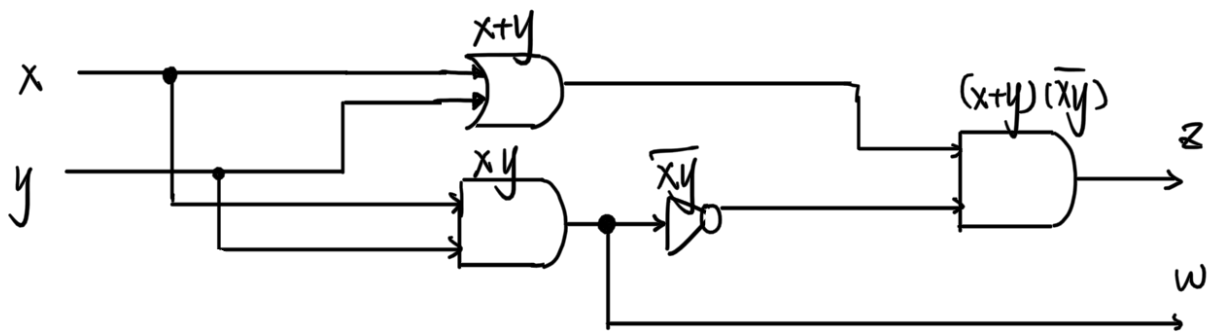

12. Use a K-map to find a minimal expansion as a Boolean sum of Boolean products of each of these functions in the variables  $x$ ,  $y$ , and  $z$ .

a)  $\overline{x}yz + \overline{x}\overline{y}z$

b)  $xyz + xy\overline{z} + \overline{x}yz + \overline{x}y\overline{z}$

c)  $xy\overline{z} + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}z$

d)  $xyz + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}y\overline{z} + \overline{x}\overline{y}\overline{z}$

12.4 ex.12

c)  $F = \bar{x}z + \bar{y}z + x\bar{z}$

|           | $yz$ | $y\bar{z}$ | $\bar{y}z$ | $\bar{y}\bar{z}$ |
|-----------|------|------------|------------|------------------|
| $x$       |      | 1          | 1          | 1                |
| $\bar{x}$ | 1    |            |            | 1                |

d)  $F = x\bar{y} + x\bar{z} + yz$

|           | $yz$ | $y\bar{z}$ | $\bar{y}z$ | $\bar{y}\bar{z}$ |
|-----------|------|------------|------------|------------------|
| $x$       | 1    |            | 1          | 1                |
| $\bar{x}$ | 1    | 1          | 1          |                  |

14. Use a K-map to find a minimal expansion as a Boolean sum of Boolean products of each of these functions in the variables  $w, x, y$ , and  $z$ .

a)  $wxyz + wx\bar{y}z + wx\bar{y}\bar{z} + w\bar{x}y\bar{z} + w\bar{x}\bar{y}z$

b)  $wxy\bar{z} + wx\bar{y}z + w\bar{x}yz + \bar{w}x\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}z$

c)  $wxyz + wxy\bar{z} + wx\bar{y}z + w\bar{x}\bar{y}z + w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}z$

d)  $wxyz + wxy\bar{z} + wx\bar{y}z + w\bar{x}yz + w\bar{x}y\bar{z} + \bar{w}xyz + \bar{w}\bar{x}yz + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}z$

12.4 ex. 14.

c)

|                  | $yz$ | $y\bar{z}$ | $\bar{y}z$ | $\bar{y}\bar{z}$ |
|------------------|------|------------|------------|------------------|
| $wx$             | 1    | 1          |            | 1                |
| $w\bar{x}$       |      |            | 1          | 1                |
| $\bar{w}x$       |      | 1          |            | 1                |
| $\bar{w}\bar{x}$ |      |            |            | 1                |

$$F = \bar{y}z + w\bar{x}y + wx\bar{y} + \bar{w}x\bar{y}\bar{z}$$

d

|                  | $yz$ | $y\bar{z}$ | $\bar{y}z$ | $\bar{y}\bar{z}$ |
|------------------|------|------------|------------|------------------|
| $wx$             | 1    | 1          |            | 1                |
| $w\bar{x}$       | 1    | 1          |            |                  |
| $\bar{w}x$       | 1    | 1          |            | 1                |
| $\bar{w}\bar{x}$ | 1    |            |            |                  |

$$F = \bar{w}x\bar{z} + wx\bar{z} + wx\bar{y} + y\bar{z} + \bar{x}y$$

24. Use the Quine–McCluskey method to simplify the sum-of-products expansions in Example 4.

**EXAMPLE 4** Use K-maps to simplify these sum-of-products expansions.

(a)  $wxyz + wxy\bar{z} + wx\bar{y}\bar{z} + w\bar{x}yz + w\bar{x}\bar{y}z + w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}\bar{x}yz + \bar{w}\bar{x}\bar{y}\bar{z}$

(b)  $wx\bar{y}\bar{z} + w\bar{x}yz + w\bar{x}y\bar{z} + w\bar{x}\bar{y}z + \bar{w}x\bar{y}\bar{z} + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z}$

(c)  $wxy\bar{z} + wx\bar{y}\bar{z} + w\bar{x}yz + w\bar{x}y\bar{z} + w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}x\bar{y}\bar{z} + \bar{w}x\bar{y}\bar{z} + \bar{w}\bar{x}yz + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z}$

12.4 ex 24.

|    |   |                                |      |       |                         |      |           |                  |         |
|----|---|--------------------------------|------|-------|-------------------------|------|-----------|------------------|---------|
| b) | 1 | $w\bar{x}yz$                   | 1011 | (1,3) | $w\bar{x}y$             | 101- | (2,5,4,7) | $\bar{y}\bar{z}$ | - - 00  |
|    | 2 | $wxy\bar{z}$                   | 1100 | (2,4) | $w\bar{y}\bar{z}$       | 1-00 | (3,6,4,7) | $\bar{x}\bar{z}$ | - 0 - 0 |
|    | 3 | $w\bar{x}y\bar{z}$             | 1010 | (2,5) | $x\bar{y}\bar{z}$       | -100 |           |                  |         |
|    | 4 | $w\bar{x}\bar{y}\bar{z}$       | 1000 | (3,4) | $w\bar{x}\bar{z}$       | 10-0 |           |                  |         |
|    | 5 | $\bar{w}x\bar{y}\bar{z}$       | 0100 | (3,6) | $\bar{x}\bar{y}\bar{z}$ | -010 |           |                  |         |
|    | 6 | $\bar{w}\bar{x}\bar{y}\bar{z}$ | 0010 | (4,7) | $\bar{x}\bar{y}\bar{z}$ | -000 |           |                  |         |
|    | 7 | $\bar{w}x\bar{y}\bar{z}$       | 0000 | (5,7) | $\bar{w}\bar{y}\bar{z}$ | 0-00 |           |                  |         |
|    |   |                                |      | (6,7) | $\bar{w}\bar{x}\bar{z}$ | 00-0 |           |                  |         |

$wxy\bar{z}$   $w\bar{x}yz$   $w\bar{x}\bar{y}\bar{z}$   $w\bar{x}\bar{y}\bar{z}$   $\bar{w}x\bar{y}\bar{z}$   $\bar{w}x\bar{y}\bar{z}$   $w\bar{x}\bar{y}\bar{z}$

$w\bar{x}y$                        $x$                        $x$

$\bar{y}\bar{z}$      $x$      $x$                        $x$

$\bar{x}\bar{z}$                                        $x$                        $x$                        $x$

$$F = \bar{y}\bar{z} + \bar{x}\bar{z} + w\bar{x}y$$

In Exercises 30–32 find a minimal sum-of-products expansion, given the K-map shown with *don't care* conditions indicated with *ds*.

32.

|                  | $yz$ | $y\bar{z}$ | $\bar{y}\bar{z}$ | $\bar{y}z$ |
|------------------|------|------------|------------------|------------|
| $wx$             |      | $d$        | $d$              | $1$        |
| $w\bar{x}$       | $d$  | $d$        | $1$              | $d$        |
| $\bar{w}\bar{x}$ |      |            |                  |            |
| $\bar{w}x$       | $1$  | $1$        | $1$              | $d$        |

12.4 ex32.

$$F = \bar{w}x + w\bar{y}$$

\*6. Let  $V = \{S, A, B, a, b\}$  and  $T = \{a, b\}$ . Find the language generated by the grammar  $(V, T, S, P)$  when the set  $P$  of productions consists of

- a)  $S \rightarrow AB, A \rightarrow ab, B \rightarrow bb.$
- b)  $S \rightarrow AB, S \rightarrow aA, A \rightarrow a, B \rightarrow ba.$
- c)  $S \rightarrow AB, S \rightarrow AA, A \rightarrow aB, A \rightarrow ab, B \rightarrow b.$
- d)  $S \rightarrow AA, S \rightarrow B, A \rightarrow aaA, A \rightarrow aa, B \rightarrow bB, B \rightarrow b.$
- e)  $S \rightarrow AB, A \rightarrow aAb, B \rightarrow bBa, A \rightarrow \lambda, B \rightarrow \lambda.$



13.1 ex. 6

$$a) S \Rightarrow AB \Rightarrow abB \Rightarrow abbb \\ L(G) = \{abbb\}$$

$$b) S \Rightarrow AB \Rightarrow aB \Rightarrow aba \\ S \Rightarrow aA \Rightarrow aa \\ L(G) = \{aba, aa\}$$

16. Construct phrase-structure grammars to generate each of these sets.

✓ a)  $\{1^n \mid n \geq 0\}$   
c)  $\{(11)^n \mid n \geq 0\}$

✓ b)  $\{10^n \mid n \geq 0\}$

13.1 ex. 1b a)  $G = \{V, T, S, P\}$  where  $V = \{S, 1\}$   
 $P = \{S \rightarrow 1S, S \rightarrow \lambda\}$   $T = \{1\}$

b)  $G = \{V, T, S, P\}$  where  $V = \{S, 0, 1, A\}$   $T = \{0, 1\}$   
 $P = \{S \rightarrow 1A, A \rightarrow 0A, A \rightarrow \lambda\}$

32. Give production rules in Backus–Naur form for the name of a person if this name consists of a first name, which is a string of letters, where only the first letter is uppercase; a middle initial; and a last name, which can be any string of letters.

### 13.1 ex.32

$\langle \text{name} \rangle ::= \langle \text{first name} \rangle \langle \text{middle initial} \rangle \langle \text{last name} \rangle$

$\langle \text{first name} \rangle ::= \langle \text{uppercase letter} \rangle \langle \text{remainder letter} \rangle | \langle \text{uppercase letter} \rangle$

$\langle \text{remainder letter} \rangle ::= \langle \text{lowercase letter} \rangle \langle \text{remainder letter} \rangle | \langle \text{lowercase letter} \rangle$

$\langle \text{uppercase letter} \rangle ::= A | B | \dots | Z$

$\langle \text{lowercase letter} \rangle ::= a | b | \dots | z$

$\langle \text{middle initial} \rangle ::= A | B | \dots | Z$

$\langle \text{last name} \rangle ::= \langle \text{lowercase letter} \rangle \langle \text{last name} \rangle | \langle \text{lowercase letter} \rangle$